

OBJECTIVE:

study of binary subtractors

A. Half subtractor

B. full subtractor

THEORY:

SUBTRACTOR

A subtractor can be designed using the same approach as that of an adder. The arithmetic operation, subtraction of two binary digits has four possible elementary operations namely,

$$0 - 0 = 0$$

$$0 - 1 = 1 \quad \text{with borrow 1}$$


$$1 - 0 = 1$$

$$1 - 1 = 0$$

in all operations, each subtrahend bit is subtracted from minued bit. in case of the second operation the minued bit is smaller than the subtracted bit, hence 1 is borrowed.

HALF SUBTRACTOR

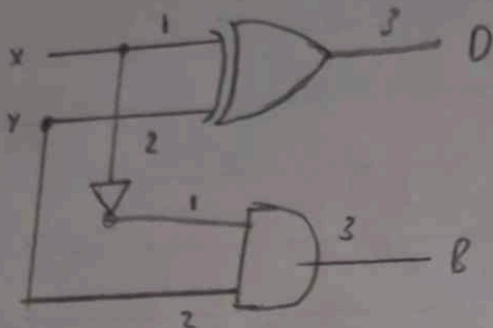A Combinational circuit which performs the subtraction of two bits is called half subtractor. This input variables designate the minued & the subtrahend bit, whereas the output variables produce the difference & borrow bits.



Input 1	Input 2	Diff	Borrow
X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

FULL SUBTRACTOR

A full-subtractor is a combinational circuit that performs a subtraction between two bits, taking into account that a 1 may have been borrowed by a lower significant stage.

A. HALF SUBTRACTOR


EQUIPMENT NEEDED

Components	Quantity
① IC 7408 2 input AND gate	1
② IC 7486 2 input XOR gate	1
③ IC 7404 NOT gate	1

PROCEDURE

When switch is pressed it indicates switch is in "HIGH" position.
When switch is unpressed it indicates switch is in "LOW" position.

- ① Make connections on bread board as shown in figure.
- ② Connect +5V to pin no. 14 & GND to pin 7 of IC 7408.
IC 7486 & IC 7404,
- ③ Connect inputs X & Y to the input switches 10 & 11, respectively
- ④ Connect difference (D) & Borrow (B) to 00 & 01 of 10 bit led indicator, respectively
- ⑤ Switch ON the kit.
- ⑥ Set the input switches S0 & S1 initially to low position.
- ⑦ Observe outputs D & B on LED L0 & L1 of 10 bit LED indicator, respectively
- ⑧ Observe the truth table for different input combinations

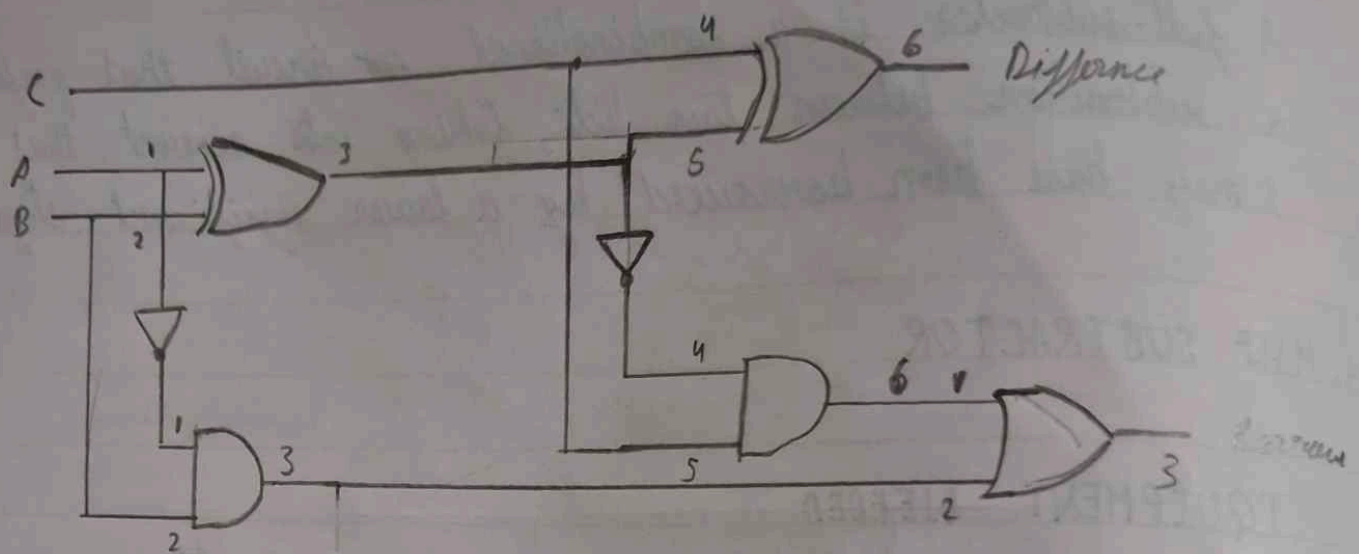

Input 1			Output 1	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0
			1	1

⑨ Verify truth table

B. FULL SUBTRACTOR

EQUIPMENT NEEDED

Component	Quantity
① IC 7408 2 input AND gate	1
② IC 7432 2 input OR gate	1
③ IC 7486 2 input XOR gate	1
④ IC 7404 NOT gate	1

PROCEDURE

- ① Make connections on bread board as shown in figure.
- ② Connect +5V to pin no 14 & the GND to pin no 7 of IC 7408, 7432, 7486, 7404
- ③ Connect inputs A, B, C the input switches
- ④ Connect Difference (D) & Borrow (B) to 00 & 01 of 10 bit led indicator, respectively.
- ⑤ Switch ON the kit
- ⑥ Set the input switches S0, S1 & S2 initially to low position.
- ⑦ Observe outputs D & B on LED L0 & L1 of 10 bits LED display, respectively.
- ⑧ Observe the output for different input combination as shown in truth table.
- ⑨ Truth Table

OBSERVATION AND RESULT:

Subtractors are studied & truth tables verified

Conclusion :

subtractions studied & truth table verified

Assessment of the Experiment / Assignment :

Timely Submission (07)	Presentation (06)	Understanding (12)	Total (25)	Signature of Teacher with date
07	06	11	24	EPD 9/9/24