

EXPERIMENT - 8

33

OBJECTIVE

To Study and test DAC-0808 circuit.

THEORY

A Digital-To-Analog Converter (DAC) transforms digital data into an analog signal. The DAC-0808 is an 8-bit DAC that converts inputs (0-255) into a proportional output voltage, commonly used in audio systems, signal processing, & control applications.

PROCEDURE

Connect +5v, +15v, -15v, & GND from Main Board to Experimental Board.

Supply (+/-12v) for Op-Amp is internally provided

supply (+5v, GND) for the circuit is internally provided

The Amplifier circuit is internally provided to this circuit DAC using Op-Amp 741

Let us assume,

When LED glows it indicates logic HIGH or 1.

When LED doesn't glow it indicates logic LOW or 0.

When input switch is unpressed it indicates switch is in 'L' position

When input switch is pressed it indicates switch is in 'H' position.

D7 S8	D6 S7	D5 S6	D4 S5	D3 S4	D2 S3	D1 S2	D0 S1	Voltz (T1) OPM
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0.668
0	0	1	0	0	0	0	0	1.34
0	1	0	0	0	0	0	0	2.68
1	0	0	0	0	0	0	0	5.35
1	1	0	0	0	0	0	0	8
1	1	1	0	0	0	0	0	9.36
1	1	1	1	0	0	0	0	9.95
1	1	1	1	1	1	1	1	10.46

Connect +5v, +12v, -12v, and GND from Power Supply to Experiment Board.

Supply (+5-12v) for Op-amp is internally provided.
Supply (+5v, GND) for the circuit is internally provided.
The amplifier circuit is internally provided in the circuit board using Op-amp 741.

Let us assume:
When LED glows it indicates logic HIGH or 1.
When LED doesn't glow it indicates logic LOW or 0.
When input switch is depressed it indicates output is 1.
When input switch is released it indicates output is 0.

- 1) Connect the AC Supply to the kit
- 2) Connect $O0$ to $I1$, $O1$ to $I2$, $O2$ to $I3$... & $O7$ to $I8$.
- 3) Connect $(V+)$ of DPM-1 on main board to pin 6 of IC 741 & $(V-)$ of DPM-1 on main board to GND of experimental board. Select range $20V$ with the help of selector switch sws
- 4) Connect fixed supplies $+5V$, GND, $+15V$, & $-15V$, from main board to $+5V$, GND, $+12V$, & $-12V$ of the module, respectively.
- 5) Set the input switches $S1-S6$ initially to 'L' position.
- 6) Switch ON the power supply of main board.
- 7) Observe the output at pin no 6 of IC 741 of Experimental Board on DPM-1,
- 8) Switch $S1$ to 'H' position.
- 9) Measure the output at pin 6 of IC 741. Similarly keep $S2$ & $S3$... $S8$ and note down the voltage (on DPM-1) at pin 6 of IC 741.
- 10) Keep all the input switches at 'H' position and note down the voltage at pin 6 of IC 741 on DPM-1.

- 11) With each Manual Pulse we can see that the values gets incremented as shown in truth table.
- 12) Instead of manual Pulse we can provide by connecting 1Hz to CLK.
- 13) Counting will be faster
- 14) Set the input switch S0 to LOW to reset counting.

Down-Counter

- 15) Set the inputs switches S1 to LOW position & S0 & S2 to High position
- 16) Observe the output at LEDs & verify truth table.
- 17) With each manual pulse we can see that the values gets decremented.
- 18) Instead of manual pulse we can provide fixed Clock by connecting 1Hz to CLK
- 19) The counting will be faster
- 20) Set the input switch S0 to LOW position to reset counting.

RESULT

DAC-0808 circuit is studied & voltage is measured using voltmeter.

INPUT					
S1	S2	LED 4	LED 3	LED 2	LED 1
L	H	H	H	H	H
L	H	H	H	H	L
L	H	H	H	L	H
L	H	H	H	L	L
L	H	H	L	H	H
L	H	H	L	H	L
L	H	H	L	L	H
L	H	H	L	L	L
L	H	L	H	H	H
L	H	L	H	H	L
L	H	L	H	L	H
L	H	L	H	L	L
L	H	L	L	H	H
L	H	L	L	H	L
L	H	L	L	L	H
L	L	L	L	L	L

Conclusion :

DAC-0808 circuit is studied & voltage is measured using
voltmeter

Assessment of the Experiment / Assignment :

Timely Submission (07)	Presentation (06)	Understanding (12)	Total (25)	Signature of Teacher with date
07	06	11	24	Dr. A. J. 21/10/24